



Bio-ExG: Multi-biosignal Amplifier System design 01



Upside Down Labs

The origin of awesome open-source hardware and software!

26 followers New Delhi, INDIA <http://upside-downlabs.tech>



www.crowdsupply.com/upside-down-labs/bioamp-exg-pill




Category Bioelectronics Version 1.0b Intro YouTube Support Project Crowd Supply Documentation hackaday.io PCB OSH Park


BioAmp EXG Pill is a small (2.54 X 1.00 cm) and elegant Analog Front End (AFE) board for BioPotential signal acquisition that you can use with any 5v Micro Controller Unit (MCU) with an ADC. It is capable of recording publication grade BioPotential signals like ECG, EMG, EOG, and EEG without the inclusion of any dedicated Hardware/Software filter, see [BioAmp EXG Pill v0.7 intro video](#) for more info. The v1.0 of BioAmp EXG pill provides even more flexibility with configuration option for Gain, BandPass, Filter, and Electrodes.



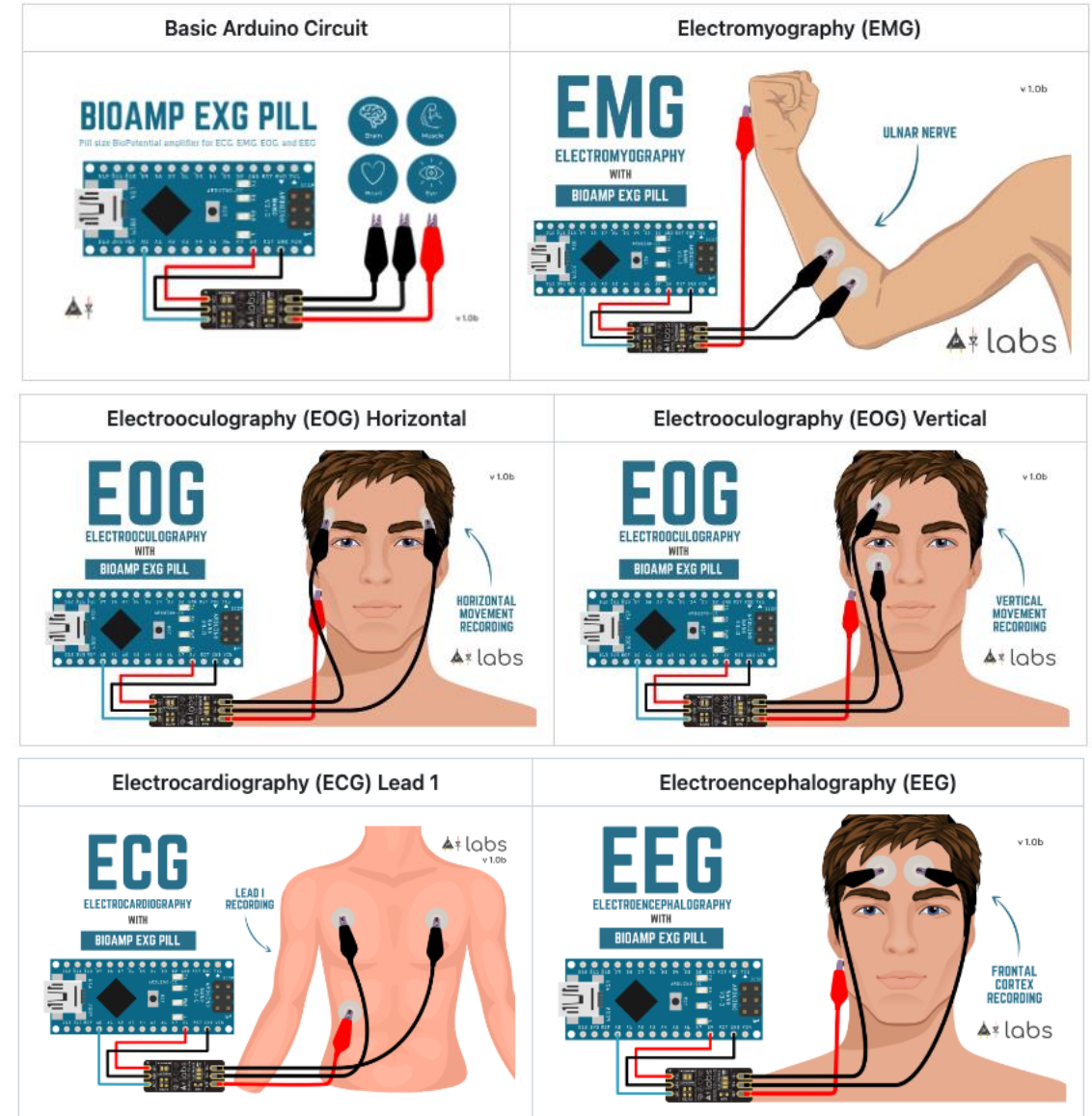BioAmp EXG Pill is a small and elegant Analog Front End (AFE) board for BioPotential signal acquisition



❑ (a) Pre-Amplifier(IA)

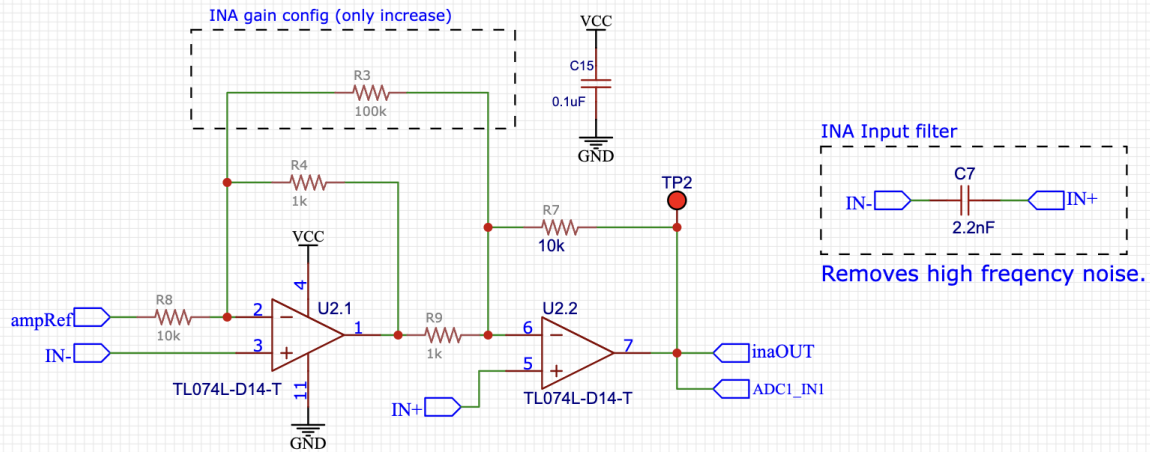

Create solder joint on J3 to narrow the Band Pass frequency range
Default: Wide input frequency band, use when recording EMG, EOG
Configured: Narrow input frequency band, use for EEG, EOG, and ECG


*** Problem Statements:**

1. 증폭단(Pre-amplifier)의 주파수에 따른 Gain/Phase 응답은 어떻게 측정할 수 있는가?
2. 이론적으로 예측한 Frequency response와 실제로 측정한 결과와의 비교는 어떻게 되는가?
3. R3저항의 영향은 무엇인가? 실제 측정한 결과를 기반으로 비교해 보자.


(주어진 회로에 대하여 회로 방정식을 세우고 분석한 결과를 반드시 포함시키기 바람.)

❑ (b) Filtering and Post-Amplifier

1000x Gain (Bandpass)

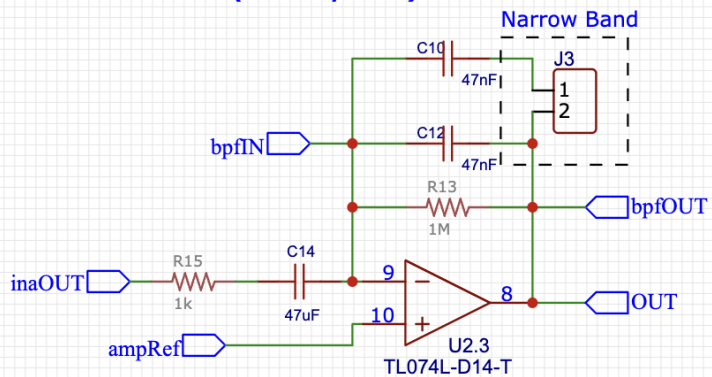

Band Pass Filter Configuration (BPFC)

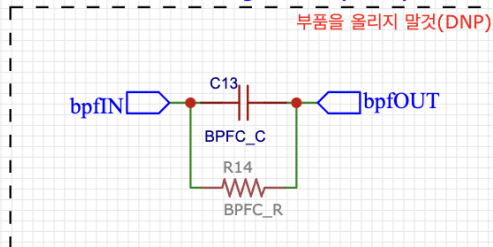

- * C8 (BPFC_C) & R3 (BPFC_R) on the back side of the PCB can be used to configure the bandpass filter.
- * Use them to configure output Gain (decrease) & Band (frequency range).